

- Derive output equations and simplify it if possible
From the truth table, derive the boolean expressions for each output. Simplify the boolean expression using boolean algebra rules, K-map method etc. The goal is used to reduce the number of logic gates required, minimizing the circuit's complexity.

- Draw logic circuit diagram

Select appropriate logic gates based on the simplified boolean expressions. Create a diagram using chosen logic gates to represent the simplified boolean expressions.

March - April 2023

Group - A

Brief Answer Questions

(10 × 1 = 10)

1) What is digital system?

⇒ Digital system is an electronic system that works with discrete values represented by 0 (low or off) and 1 (high or on) and store data in the form of binary bit.

2) How many different combination can be represented by 5-bit binary data?

⇒ $2^5 = 32$.


In 32 different combination, 5-bit binary data can be represented.

3) What is the use of Karnaugh Map?

⇒ The use of Karnaugh Map is to simplify the boolean expression and reducing logic circuits. This leads in reducing the size and complexity of digital circuit.

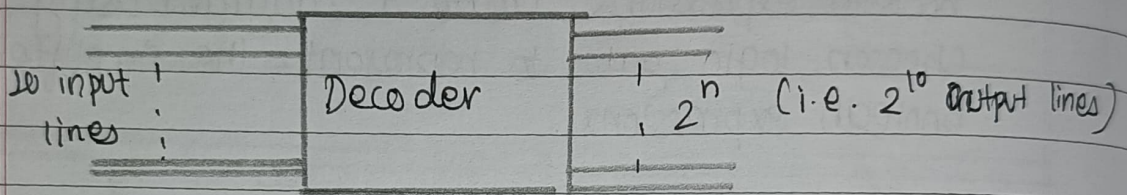4) How many input lines are required to generate 995 decoded lines?

⇒ $2^{10} \geq 995$. Therefore, 10 input lines are required to generate 995 decoded lines.



5) Differentiate between combinational and sequential circuit.

⇒

Combinational circuits	Sequential circuit
• They are time independent circuits which do not depend upon previous inputs to generate any output. • It is easy to use and handle.	• They are dependent to clock cycles and depend upon present as well as past inputs to generate any output. • It is not easy to use and handle.

6) What is the problem of "T" flip-flop.

⇒ The T-flip flop can only store a single bit of information and cannot perform more complex operations. It produces noise on the input signal.

7) What is the number of clock pulses required to input and output "5" bit data in parallel in serial out shift register?

⇒ The number of clock pulse required to input and output "5" bit data in parallel in serial out shift register are 6. One is to load and five to shift out.

8) Define don't care condition.

⇒ In K-Map, each min-term is represented by 1 and max-term with 0. A situation where we cannot differentiate 1 and 0, such situation is called don't care condition.

9) How many don't care conditions are possible in 8×3 encoder?

⇒ $2^8 - 8 = 248$ don't care conditions are possible in 8×3 encoder.

10) Why flip flop is said to be 1 bit memory?

⇒ Flip-flop is said to be 1 bit memory because it can store a single binary digit (0 or 1) and retains that data until it is changed by a control signal.

Group-B

Short answer questions (Any Five)

(5x3=15)

11) Convert $(2A3B.2A)_{16}$ into binary, octal and decimal.

⇒

• Converting to Binary


$$(2A3B.2A)_{16} \rightarrow (?)_8$$

$$\Rightarrow (001010101000111011.00101010)_2$$

$$\Rightarrow (0010101000111011.00101010)_2$$

• Converting to Octal

$$(0010101000111011.00101010)_2$$

 

$$\Rightarrow (025073.124)_8$$

• Converting to Decimal

$$(2A3B.2A)_{16} \rightarrow (?)_{10}$$

$$= 2 \times 16^3 + A \times 16^2 + 3 \times 16^1 + B \times 16^0 + 2 \times 16^{-1} + A \times 16^{-2}$$

$$= (10811.16406)_{10}$$


12) Realize the property of AND, OR and NOT gate using NAND gate.

⇒


• AND Gate




NAND Gate

 


• OR Gate

 

NAND Gate

 

• NOT Gate

 

NAND Gate



13) If a Boolean functions $F = \bar{x}y + x\bar{y} + xyz$, Solve the given functions using K-map.

⇒


$$F = \bar{x}y + x\bar{y} + xyz$$

F		yz			
x		$\bar{y}\bar{z}$	$\bar{y}z$	yz	$y\bar{z}$
$\bar{x}$				1	1
x		1	1	1	

$$\therefore F = \bar{x}y + x\bar{y} + yz$$

14) Design 4x1 multiplexer.

⇒

 


Operational Table

Selection		Output
S_1	S_0	F
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

$$F = I_0 \bar{S}_1 \bar{S}_0 + I_1 \bar{S}_1 S_0 + I_2 S_1 \bar{S}_0 + I_3 S_1 S_0$$

Logic Circuit Diagram

 

15)

Explain triggering of a flip-flop with its types.

⇒

The state of flip-flop is changed by a momentary change in the input signal. This change is called a trigger. Triggering is the way of activating a flip-flop so that it can respond to the inputs and can update its output state as per the input data. Its types are:


• Edge-Triggered

A flip flop that changes its output state only at a moment of a transition from one logic level to another. Its types are:

i) Positive edge triggered:

It changes state on the rising edge.


For example:

 

ii) Negative edge triggered:

It changes state on the falling edge.

For example:

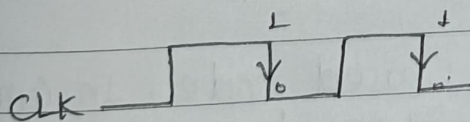

16) If a Boolean function $F = AB + \bar{B}C$, find an equivalent POS.

⇒

$$F = AB + \bar{B}C$$

$$\bar{F} = \overline{AB + \bar{B}C}$$

$$\bar{F} = \bar{A}\bar{B} \cdot B\bar{C} \quad [\text{Using De-morgan's theorem}]$$

$$\bar{F} = \bar{A} + \bar{B} \cdot B + \bar{C}$$

$$\therefore \bar{F} = (\bar{A} + \bar{B}) \cdot (B + \bar{C})$$

Finding SOP from F' .

$$F = \overline{\bar{F}}$$

$$= \overline{[(\bar{A} + \bar{B}) \cdot (B + \bar{C})]}$$

$$= \overline{\bar{A} + \bar{B}} + \overline{B + \bar{C}}$$

$$= (A \cdot B) + (\bar{B} \cdot C)$$

∴ The equivalent POS from boolean function

$$F = \bar{A}B + \bar{B}C \text{ is } F = AB + \bar{B}C \text{ is } (\bar{A} + \bar{B}) \cdot (B + \bar{C})$$

Group-C

Long Answer Questions (Any three)

(3x5 = 15)

17) What is gray code? Design 3-bit synchronous counter.

⇒ Gray code is a transition based code. In Gray code, all one bit is interchanged during the transition in a sequence from previous transition.

3-bit Synchronous counter

 


Fig: State Diagram

State Table

Present state			Next state			Flip-Flop input		
x	y	z	x	y	z	Tx	Ty	Tz
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

$$T_x$$

	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz
$\bar{x}$			1	
x			1	

$$\therefore T_x = yz$$

$$T_y$$


	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz
$\bar{x}$		1	1	
x		1	1	

$$\therefore T_y = z$$

$$T_z$$

	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz
$\bar{x}$	1	1	1	1
x	1	1	1	1


$$\therefore T_z = 1$$

 Logic Circuit Diagram

- 18) You are provided with data bits 1011. The register provided has the capability to store all bits in one clock pulse and can be retrieved those stored bits only one at a time, from right most flip flop. Your work is to draw the circuit and show all necessary steps to store and retrieve the provided data in provided register.

⇒

Logic Circuit Diagram

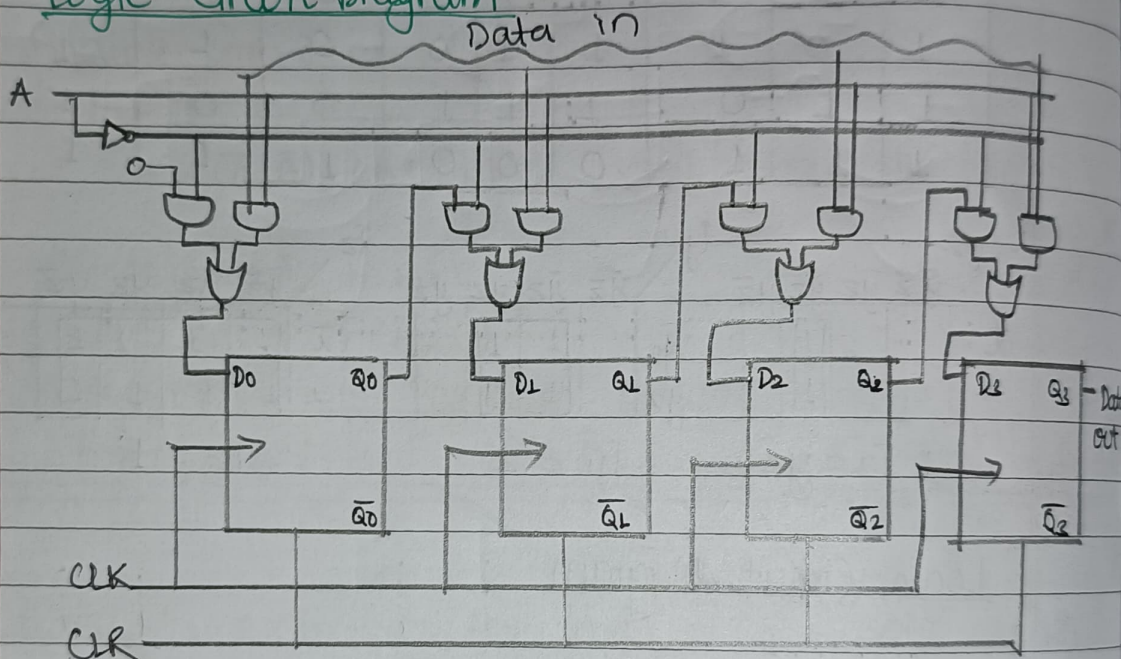

$A=1$ Data in parallelly

$A=0$ Data out parallelly

Operational Table


Clock	A	Q ₀	Q ₁	Q ₂	Q ₃
0	X	0	0	0	0
1	1	1	0	1	1
1	0	0	1	0	1
1	0	0	0	1	0
1	0	0	0	0	1
1	0	0	0	0	0
0	0				

→ Initially clear state


→ Data in parallelly

1
1
0
1

→ Data out serially

 Timing Diagram

 
19) Design a circuit diagram of a 3-bit parallel adder.



$$S = A \oplus B \oplus C$$

$$C = C(A \oplus B) + AB$$

Logic Circuit Diagram

 


20) What ~~are~~ is the advantage of JK flip flop over clocked SR flip flop? Explain the operational characteristics of JK flip flop with logic diagram.

⇒ The advantage of J-K Flip-Flop over clocked S-R Flip-Flop are:

- It is faster than S-R flip flop.
- JK Flip-Flop has a feedback path.
- JK Flip-Flop doesn't have indeterminate state.
i.e. it works when both input are one)

Logic Circuit Diagram

 

Characteristics Table

clock	J	K	Qp	Qn
0	X	X	X	No change
1	0	0	0	0
L	0	0	1	1
L	0	1	0	0
L	0	1	1	0
L	1	0	0	1
L	1	0	1	1
L	1	1	0	1
1	1	1	1	0

Characteristics Equation


Qn

	$\bar{K}\bar{A}P$	$\bar{K}AP$	KAP	$K\bar{A}\bar{P}$
J		1		
$\bar{J}$	1	1		1

$$\therefore Q_n = J\bar{Q}P + \bar{K}QP$$

Excitation Table

Present state Q_p	Next state Q_n	FF input	
		J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

 Timing Diagram

Group-D comprehensive Answer

(2x10 = 20)

21) What is Boolean algebra? List any five Boolean rules and verify any two Boolean rules using truth table method.

⇒ Boolean algebra is a mathematical tool for designing and analyzing digital circuits. Some five Boolean rules are:

- Commutative Law

$$A + B = B + A$$

$$A \cdot B = B \cdot A$$

- Associative Law

$$A + (B + C) = (A + B) + C$$

$$A \cdot (B \cdot C) = (A \cdot B) \cdot C$$

- Distributive Law

$$A + (B \cdot C) = (A + B) \cdot (A + C)$$

$$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$$

- De Morgan's Law

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

- Identity Law

$$A \cdot 1 = A$$

$$A + 0 = A$$

De-Morgan's Law

① $\overline{A+B} = \bar{A} \cdot \bar{B}$

A	B	A+B	$\overline{A+B}$	$\bar{A}$	$\bar{B}$	$\bar{A} \cdot \bar{B}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

$\therefore \overline{A+B} = \bar{A} \cdot \bar{B}$

② $\overline{A \cdot B} = \bar{A} + \bar{B}$

A	B	A.B	$\overline{A \cdot B}$	$\bar{A}$	$\bar{B}$	$\bar{A} + \bar{B}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

$\therefore \overline{A \cdot B} = \bar{A} + \bar{B}$

Distributive Law

① $A + (B \cdot C) = (A+B) \cdot (A+C)$

A	B	C	$B \cdot C$	$A+B$	$A+C$	$A+(B \cdot C)$	$(A+B) \cdot (A+C)$
0	0	0	0	0	0	0	0
0	0	1	0	0	1	0	0
0	1	0	0	1	0	0	0
0	1	1	1	1	1	1	1
1	0	0	0	1	1	1	1
1	0	1	0	1	1	1	1
1	1	0	0	1	1	1	1
1	1	1	1	1	1	1	1

$$\therefore A+(B \cdot C) = (A+B) \cdot (A+C)$$

$$\textcircled{2} A(B+C) = (A \cdot B) + (A \cdot C)$$

A	B	C	$B+C$	$A \cdot B$	$A \cdot C$	$A(B+C)$	$(A \cdot B) + (A \cdot C)$
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	0	1	1	1
1	1	0	1	1	0	1	1
1	1	1	1	1	1	1	1

$$\therefore A(B+C) = (A \cdot B) + (A \cdot C)$$

22) Differentiate between PLA and ROM. Design MOD-150 asynchronous counter.

⇒ The difference between PLA and ROM are as follows:

Basis	PLA	ROM
1) Full Form	Programmable Logic Array.	Read Only Memory
2) Functionality	Implements logic functions using programmable AND and OR gates.	Stores data and doesn't perform logic function.
3) Configurability	Both AND and OR arrays are configurable.	Only the OR gates array is configurable.
4) Flexibility	Can accommodate future logic changes due to its reprogrammability.	Cannot be updated, modified are or replaced unless, specifically required to update data.
5) Cost and manufacturing	Manufacturing costs could increase due to initial programming.	No initial programming required, potentially lower cost.
6) Usability	It is more convenient to use.	It is less convenient as compared to PLA where don't care condition is excessive.

7) Block Diagram

MOD-150 asynchronous Counter


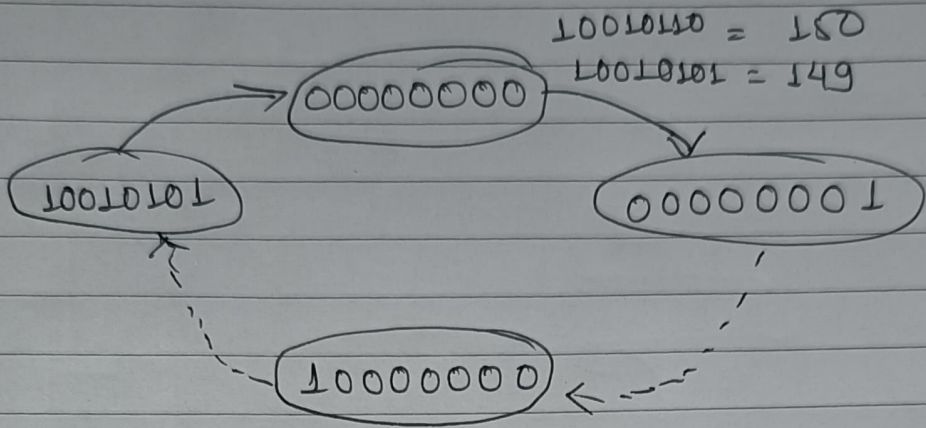


Fig: State Diagram

Logic Circuit Diagram

 

Operational Table

Clock	Q ₇	Q ₆	Q ₅	Q ₄	Q ₃	Q ₂	Q ₁	Q ₀
0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	1
⋮	⋮	⋮	⋮	⋮	⋮	⋮	⋮	⋮
149	1	0	0	1	0	1	0	1
150	0	0	0	0	0	0	0	0