
 



Half Subtractor

 


Full Subtractor




Experiment Diagram of 4*2 Encoder

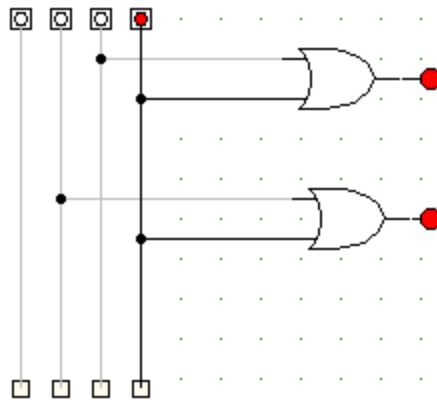


Experiment Diagram of 2*4 Decoder

 


Experiment of 4*1 MUX

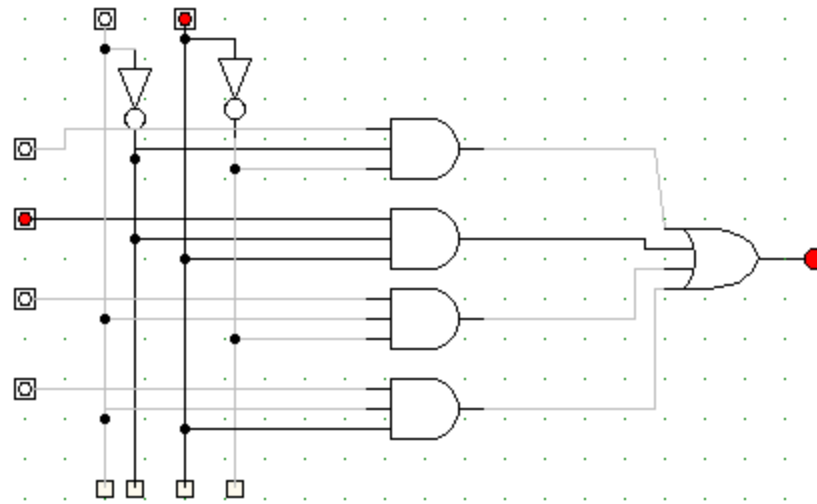


Experiment of 1*4 De-Mux

 

 
Experiment of 3 bit (mod 8) synchronous up counter



 
Experiment of 3 bit (mod 8) asynchronous up counter




Experiment of 3 bit SISO shift register

 


Experiment of 3 bit SIPO shift register

 

Experiment of 3 bit PIPO shift register

 

Experiment of 3 bit PISO shift register

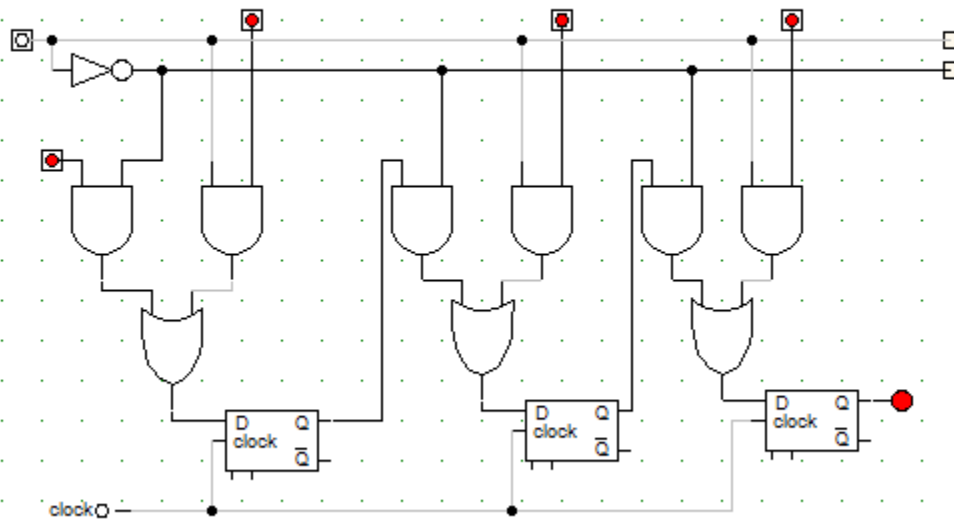

Bi-Directional Shift Register

